

**JoVE: Science Education**  
**Single-Phase Rectifiers**  
--Manuscript Draft--

<b>Manuscript Number:</b>	10257
<b>Full Title:</b>	Single-Phase Rectifiers
<b>Article Type:</b>	Manuscript
<b>Section/Category:</b>	Manuscript Submission
<b>Corresponding Author:</b>	Ali Bazzi  UNITED STATES
<b>Corresponding Author Secondary Information:</b>	
<b>Corresponding Author's Institution:</b>	
<b>Corresponding Author's Secondary Institution:</b>	
<b>First Author:</b>	Ali Bazzi
<b>First Author Secondary Information:</b>	
<b>Order of Authors:</b>	Ali Bazzi
<b>Order of Authors Secondary Information:</b>	

**PI:** Ali Bazzi – University of Connecticut

**Electrical Engineering Science Education Title:** Single-Phase Rectifiers

### **Overview:**

The objective of this experiment is to study half-wave and full-wave single-phase rectifier operation for different load types. Rectification along with the turn-off characteristics of diodes are observed when the diode current reaches zero. Filtering the DC output voltage using an electrolytic capacitor is also studied.

**ATTENTION:** During this experiment, do not touch any part of the circuit while energized. The AC source is only grounded as shown in Figures 1 and 2 when the function generator is a source. Do NOT ground the VARIAC.

### **Principles:**

Diode rectifiers are two-terminal semiconductor devices that pass current in one direction and block it in the other direction. Current passes from the anode to the cathode but not from the cathode to the anode. There is typically some leakage current in the blocking direction (cathode to anode), but it is very low. Diodes blocking current flow thus need to block a certain voltage level across from the cathode to the anode, so diodes are rated for their current carrying capability and their voltage blocking capability. When voltage across the diode terminals exceeds that voltage blocking rating, the diode operates in the break-down region where it breaks and passes current both ways. The fact that diodes pass current in one direction leads to rectification capabilities where AC can be converted to DC.

### **Procedure:**

1. For this experiment, two AC sources are used for different parts, a variable transformer (VARIAC) at a low frequency of 60 Hz and a function generator with 10V peak sinusoidal output and 1 kHz frequency.
  - 1.1 Before you start, connect the differential probe to one scope channel, and a regular probe to the other channel.
  - 1.2 Adjust the buttons on the probes as follows: differential probe at 20X (or 1/20) and the regular probe at 10X. Do not forget to turn ON the differential probe.
  - 1.3 On each channel's menu on the scope, set the probe to be at 10X. For the differential probe, you will need to manually multiply any measurements or results by two to reach the 20X desired.
  - 1.4 To set up the function generator, make sure the  $50\Omega$  OUTPUT is connected to a BNC-to-alligator cable.
    - 1.4.1 Connect the alligator clips to a regular scope probe to observe the function generator output.
    - 1.4.2 Set your output to be a sinusoid at 10V peak and 1 kHz frequency with zero DC offset.
    - 1.4.3 Observe the function generator output and adjust its settings to achieve the desired output waveform.

1.4.4 Once your signal is set, disconnect the BNC connector but keep the function generator ON to maintain its settings. Disconnect your scope probe from the generator output.

1.5 To setup the VARIAC, make sure the VARIAC output (looks like a regular receptacle) is not connected to any cable.

- 1.5.1 Keep the VARIAC OFF and make sure its knob is set to zero.
- 1.5.2 Slowly adjust the VARIAC knob to 5% output. This should yield around 10V peak voltage as you will see later.

## 2. Half-Wave Rectifier

### 2.1 Resistive Load with High Frequency Input

- 2.1.1 Use the function generator as the AC source but keep it disconnected from the circuit for now.
- 2.1.2 On the proto board, build the circuit shown in Fig. 1. The diode ( $D$ ) is 2A01G-T rated for 50V and 2A while the load resistor ( $R$ ) is  $51\Omega$ .

  - 2.1.2.1 Make sure the diode polarity is correct. The dash on the diode is at the cathode.

- 2.1.3 Before connecting the differential probe to the circuit, tie the probe's terminals together and adjust its measured waveform on the screen to show zero offset voltage.

  - 2.1.3.1 Connect the differential voltage probe across the load resistor to observe the output voltage  $V_O$ .
  - 2.1.3.2 Connect a regular probe across the AC side to observe the input voltage  $V_{IN}$ .

- 2.1.4 Connect the function generator to the circuit.
- 2.1.5 Adjust the time base on the scope to show  $V_{IN}$  and  $V_O$  for up to four fundamental cycles of  $V_{IN}$ . Make a copy of the waveforms.

  - 2.1.5.1 Zoom in at the diode turn-off region and make a copy of the waveforms.

- 2.1.6 Disconnect your function generator and remove your differential probe for load modifications. Keep the rest of the circuit and connections as they are.

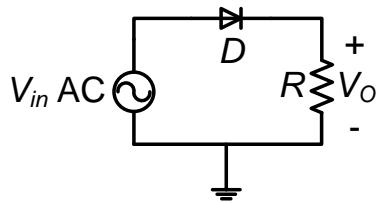


Fig. 1. Half-wave rectifier with resistive load

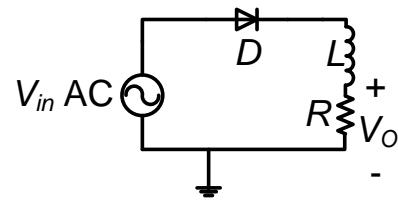


Fig. 2. Half-wave rectifier with R-L load

### 2.2 Resistive-Inductive Load with High Frequency Input

- 2.2.1 Using the same circuit in Fig. 1, connect a  $4.7\text{mH}$  inductor ( $L$ ) in series with the resistive load as shown in Fig. 2.
- 2.2.2 Connect the differential voltage probe across the load resistor to observe the resistor voltage  $V_O$  which has the same waveform shape as the R-L load current  $I_O$ .

- 2.2.3 Turn the function generator output ON.
- 2.2.4 Adjust the time base on the scope to show  $V_{IN}$  and  $V_O$  for up to four fundamental cycles of  $V_{IN}$ . Make a copy of the waveforms.
  - 2.2.4.1 Zoom in at the diode turn-off region and observe the delay in the turn-off time compared to 3.3.1. Make a copy of the waveforms.
- 2.2.5 Turn the function generator output OFF and disconnect it from the circuit.
- 2.2.6 Remove the inductor  $L$  and keep the rest of the circuit as it is.

### 2.3 Resistive Load with Low Frequency Input

- 2.3.1 Make sure the VARIAC output is at 5% and disconnected from the circuit. Connect the differential probe across the VARIAC, turn the VARIAC ON and slightly adjust its output to achieve 10 V peak.
  - 2.3.1.1 Capture the waveform on the scope to use as your reference input voltage observation.
  - 2.3.1.2 Turn the VARIAC OFF but do not change its voltage setting.
- 2.3.2 Using the same circuit from Fig. 1, i.e. with the inductor disconnected and the resistor being the only load, connect the VARIAC output using the plug-banana cable.
- 2.3.3 Connect the differential voltage probe across the load resistor to observe the output voltage  $V_O$ .
- 2.3.4 Turn ON the VARIAC output. Stay away from the circuit and observe the waveforms on the scope. If you need to debug your circuit, power the VARIAC OFF first.
- 2.3.5 Adjust the time base on the scope to show  $V_O$  for up to four fundamental cycles. Make a copy of the waveform.
  - 2.3.5.1 Zoom in at the diode turn-off region and make a copy of the waveforms.
- 2.3.6 Turn OFF the VARIAC and disassemble your circuit. Do NOT change the VARIAC voltage setting.

## 3. Full-Wave Rectifier

### 3.1 Resistive Load

- 3.1.1 On the proto board, build the circuit shown in Fig. 3.
  - 3.1.1.1 Make sure the diode polarity is correct. The dash on the diode is at the cathode.
- 3.1.2 Once your circuit is ready, connect the VARIAC output as the AC source.
- 3.1.3 Connect the differential voltage probe across the load resistor to observe the output voltage  $V_O$ .
- 3.1.4 Turn ON the VARIAC output. Stay away from the circuit and observe the waveforms on the scope. If you need to debug your circuit, power the VARIAC OFF first.
- 3.1.5 Adjust the time base on the scope to show  $V_O$  for up to four fundamental cycles of  $V_{IN}$ . Make a copy of the waveforms.
  - 3.1.5.1 Measure the peak-to-peak value of  $V_O$  by using the cursors.

3.1.6 Keep the probe connections as they are and Turn OFF the VARIAC and disassemble your circuit.

3.1.6.1 Do NOT change the VARIAC voltage setting.

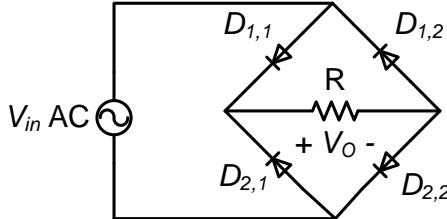


Fig. 3. Full-wave rectifier with resistive load

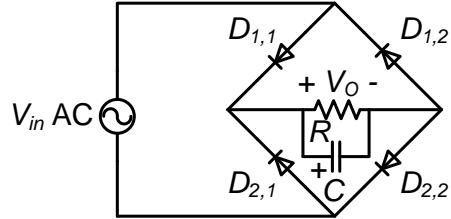


Fig. 4. Full-wave rectifier with resistive load and capacitive filtering

### 3.2 Resistive Load with Filtering Capacitor

3.2.1 Using the same circuit in Fig. 3, connect an electrolytic capacitor (C) supplied by your instructor in parallel with the resistive load as shown in Fig 4.

3.2.1.1 4. Make sure the capacitor polarity is correct with the ( — ) terminal connected to negative side of the load.

3.2.2 Turn ON the VARIAC output. Stay away from the circuit and observe the waveforms on the scope. If you need to debug your circuit, power the VARIAC OFF first.

3.2.3 Adjust the time base on the scope to show  $V_o$  for up to four fundamental cycles of  $V_{in}$ . Make a copy of the waveforms.

3.2.3.1 Measure the peak-to-peak value of  $V_o$  by using the cursors and the AC coupling option for that channel (AC coupling eliminates the DC offset of a signal).

3.2.4 Return this to DC coupling once you take your measurement.

3.2.5 Turn OFF the VARIAC.

3.2.6 Disassemble your circuit and clean up your bench.

### Representative Results:

It is expected that a resistive load coupled to a half-wave rectifier will only see the positive half-cycle of the input AC voltage since the diode rectifier can pass current in one direction. With a full bridge rectifier, the input positive and negative half cycles are rectified to be positive, but adding a capacitor will filter out most of the voltage ripple and provide the load with a clean dc voltage. When an inductor is added in series with the load, it is expected that the diode turn off will be delayed. This can be explained as follows: Diodes turn off under two conditions that are required to coexist – 1) the current in the diode has to go to zero, and the voltage across the diode (Anode-to-cathode voltage) is below the turn-on threshold. When an inductor is in series with the load, it stores energy and will act as a current source when the source is not available or is going negative at the diode's anode side. Therefore, inductor current will maintain the diode as forward biased until the inductor energy is dissipated. Essential equations that govern basic rectifier circuits with input  $v_{in}=V_0\cos(\omega t)$ :

- Single diode and resistive load:  $\langle v_{out} \rangle = V_o/\pi$

